

# Application Note AN-944

## Use Gate Charge to Design the Gate Drive Circuit for Power MOSFETs and IGBTs

### Table of Contents

	Page
1. Input behavior of a MOS-gated transistor .....	1
2. Test Circuit.....	1
3. The Gate Charge Curve.....	3
4. Beware When Comparing Different Products .....	4

Designers unfamiliar with MOSFET or IGBT input characteristics begin drive circuit design by determining component values based on the gate-to-source, or input, capacitance listed on the data sheet. RC values based on the gate-to-source capacitance normally lead to a gate drive that is hopelessly inadequate.

Although the gate-to-source capacitance is an important value, the gate-to-drain capacitance is actually more significant—and more difficult to deal with—because it is a non-linear capacitance affected as a function of voltage; the gate-to-source capacitance is also affected as a voltage function, but to a much lesser extent.

# Use Gate Charge to Design the Gate Drive Circuit for Power MOSFETs and IGBTs

Topics covered:

- *Background*
- *Test method*
- *How to interpret the gate charge curve*
- *How to estimate switching times*
- *How to compare different devices*


## 1. Input behavior of a MOS-gated transistor

Designers unfamiliar with MOSFET or IGBT input characteristics begin drive circuit design by determining component values based on the gate-to-source, or input, capacitance listed on the data sheet. RC value based on the gate-to-source capacitance normally lead to a gate drive that is hopelessly inadequate.

Although the gate-to-source capacitance is an important value, the gate-to-drain capacitance is actually more significant—and more difficult to deal with—because it is a non-linear capacitance affected as a function of voltage; the gate-to-source capacitance is also affected as a voltage function, but to a much lesser extent. This gate-to-drain capacitance function is similar to that found in vacuum tube amplifiers.

The gate-to-drain capacitance effect is akin to the “Miller” effect, a phenomenon by which a feedback path between the input and output of an electronic device is provided by the interelectrode capacitance. This affects the total input admittance of the device which results in the total dynamic input capacitance generally being greater than the sum of the static electrode capacitances. The phenomenon of the effects of the plate impedance and voltage gain on the input admittance was first studied in vacuum tube triode amplifier circuits by John M. Miller. Essentially, at high frequencies where the grid-to-plate (gate-to-drain) capacitance is not negligible, the circuit is not open but involves a capacitance that is a function of the voltage gain. Solving for the “Miller” effect is not exactly a straightforward process, even with vacuum tubes where much is known, but is even more difficult in MOSFETs. In actuality, the gate-to-drain capacitance though smaller in static value than the gate-to-source capacitance, goes through a voltage excursion that is often more than 20 times that of the gate-to-source capacity. Therefore, the gate-to-drain or “Miller” capacitance typically requires more actual charge than the input capacitance.


To account for both gate-to-source and gate-to-drain capacitance in a way readily usable by designers, International Rectifier supplies a “gate charge” specifications for its IGBTs and HEXFET POWER MOSFETs. that can be used to calculate drive circuit requirements. Gate charge is defined as the charge that must be supplied to the gate, either to swing the gate by a given amount, or to achieve full switching.

 

## 2. Test Circuit

A typical test circuit that can be used to measure the gate charge is shown in Figure 1. In this circuit, an approximately constant current is supplied to the gate of the device-under-test from the 0.1 microfarad capacitor C1, through the regulator diode D1. A constant current in the drain circuit is set by setting the voltage on the gate of HEXFET POWER MOSFET 1, so the net measurement of the charge consumed by the gate is relative to a given current and voltage in the source-to-drain path.

Figure 1. HEXFET POWER MOSFET Gate Charge Circuit.

 


**Figure 2.** Gate Charge Waveform for Different Values of Drain Voltage (IRF130:  $I_G = 1.5$  mA,  $I_D = 1$  A,  $V_{DD} = 10, 40$  and  $80$  volts).

The importance of the gate charge data to the designer is illustrated as follows. Taking the charge are required to switch a previous example, about 15 nanocoulombs of gate if 1.5 amps is supplied to the gate, the device will be drain voltage of 80 volts and a drain current of 12 amps. Since the 15 nC gate charge is the product of the gate input current and the switching time, switched in 10 nS. It follows that if 15 mA is supplied to the gate, then switching occurs in 1 ms, and so on. These simple calculations immediately tell the designer the trade-offs between the amount of current available from the drive circuit and the achievable switching time. With gate charge known, the designer can develop a drive circuit appropriate to the switching time required.

Consider a typical practical example of a 100 kHz switcher, in which it is required to achieve a switching time of 100 nanoseconds.

An oscillogram of the gate-to-source voltage during testing, shown in Figure 2, relates the gate voltage to time. Since a constant current is supplied to the gate, the horizontal time scale is directly proportional to the charge supplied to the gate. With a suitable scaling factor, therefore, this oscillogram is a plot of gate voltage versus charge. The point on the oscillogram of the second voltage rise indicates where the device is fully switched on. During the first voltage rise, the gate-to-source capacitance is charging, and during the flat portion, the gate-to-drain capacitance is charging. This oscillogram therefore clearly differentiates between the charge required for the gate-source and gate-to-drain ("Miller") capacitances. At the second voltage rise, both capacitances are charged to the extent needed to switch the given voltage and current. A more detailed explanation of the interpretation of this data is given later. The graph in Figure 3 represents gate voltage versus gate charge in nanocoulombs for an IRF130. Although the second voltage rise indicates the point at which the switching operation is completed, normal design safety margins will dictate that the level of drive voltage applied to the gate is greater than that which is just required to switch the given drain current and voltage. The total charge consumed by the gate will therefore in practice be higher than the minimum required-but not necessarily significantly so. For example, the gate charge required to switch 12 amps at 80 volts is 15 nanocoulombs (point A), and the corresponding gate voltage is about 7 volts.

If the applied drive voltage has an amplitude of 10 volts (i.e. a 3 volt margin), then the total gate charge actually consumed would be about 20 nanocoulombs, (point B). As shown on the graph, whether switching 10 volts or 80 volts in the drain circuit, there is a much less than proportional difference in the charge required. This is because the "Miller" capacitance is a nonlinear function of voltage, and decreases with increasing voltage.

 

**Figure 3.** Gate Voltage Versus Gate Charge for the IRF130.

The required gate drive current is derived by simply dividing the gate charge,  $15 \times 10^{-9}$ , by the required switching time,  $100 \times 10^{-9}$ , giving 150 mA. From this calculation, the designer can further arrive at the drive circuit impedance. If the drive circuit applies 14 volts to the gate, for instance, then a drive impedance of about 50 ohms would be required. Note that throughout the “flat” part of the switching period (Figure 3), the gate voltage is constant at about 7 volts. The difference between the applied 14 volts and 7 volts is what is available to drive the required current through the drive circuit resistance.

The gate charge data also lets the designer quickly determine average gate drive power. The average gate drive power,  $P_{\text{DRIVE}}$ , is  $Q_G V_G$ . Taking the above 100 kHz switcher as an example, and assuming a gate drive voltage  $V_G$  of 14 volts, the appropriate value of gate charge  $Q_G$  is 27 nanocoulombs (point C on Figure 3). The average drive power is therefore  $27 \times 10^{-9} \times 14 \times 10^5 = 0.038$  Watts. Even though the 150 mA drive current which flows during the switching interval may appear to be relatively high, the average power is minuscule (0.004%) in relation to the power being switched in the drain current. This is because the drive current flows for such a short period that the average power is negligible. Thus actual drive power for MOSFETs is minute compared to bipolar requirements, which must sustain switching current during the entire ON condition. Average drive power, of course, increases at higher frequencies, but even at 5 MHz it would be only 1.9W.

### 3. The Gate Charge Curve

The oscillograms of the gate-to-source voltage in Figure 2 neatly delineate between the charge required for the gate-to-source capacitance, and the charge required for the gate-to-drain, or “Miller” capacitance. The accompanying simplified test circuit and waveform diagram (Figures 4 and 5 respectively) give the explanation. Before time  $t_0$ , the switch S is closed; the device under test (DUT) supports the full circuit voltage,  $V_{\text{DD}}$ , and the gate voltage and drain current are zero. S is opened at time  $t_0$ ; the gate-to-source capacitance starts to charge, and the gate-to-source voltage increases. No current flows in the drain until the gate reaches the threshold voltage. During period  $T_1$  to  $t_2$ , the gate-to-source capacitance continues to charge, the gate voltage continues to rise and the drain current rises proportionally. So long as the actual drain current is still building up towards the available drain current,  $I_D$ , the freewheeling rectifier stays in conduction, the voltage across it remains low, and the voltage across the DUT continues to be virtually the full circuit voltage,  $V_{\text{DD}}$ . The top end of the drain-to-gate capacitance  $C_{\text{AD}}$  therefore remains at a fixed potential, whilst the potential of the lower end moves with that of the gate. The charging current taken by  $C_{\text{AD}}$  during this period is small, and for practical purposes it can be neglected, since  $C_{\text{AD}}$  is numerically small by comparison with  $C_{\text{CS}}$ .

At time  $t_2$ , the drain current reaches  $I_D$ , and the freewheeling rectifier shuts off; the potential of the drain now is no longer tied to the supply voltage,  $V_{\text{DD}}$ . The drain current now stays constant at the value  $I_D$  enforced by the circuit, whilst the drain voltage starts to fall. Since the gate voltage is inextricably related to the drain current by the intrinsic transfer characteristic of the DUT (so long as operation remains in the “active” region), the gate voltage now stays constant because the “enforced” drain current is constant. For the time being therefore, no further charge is consumed by the gate-to-source capacitance, because the gate voltage remains constant. Thus the drive current now diverts, in its entirety, into the “Miller” capacitance  $C_{\text{AD}}$ , and the drive circuit charge now contributes exclusively to discharging the “Miller” capacitance.

The drain voltage excursion during the period  $t_2$  to  $t_3$  is relatively large, and hence the total drive charge is typically higher for the “Miller” capacitance  $C_{\text{AD}}$  than for the gate-to-source capacitance  $C_{\text{CS}}$ . At  $t_3$  the drain voltage falls to a value equal to  $I_D \times R_{\text{DS(ON)}}$ , and the DUT now comes out of the “active” region of operation. (In bipolar transistor terms, it has reached “saturation.”)

The gate voltage is now no longer constrained by the transfer characteristic of the device to relate to the drain current, and is free to increase. This it does, until time  $t_4$ , when the gate voltage becomes equal to the voltage “behind” the gate circuit current source. The time scale on the oscillogram of the gate-to-source voltage is directly proportional to the charge delivered by the drive circuit, because charge is equal to the product of current and time, and the current remains constant throughout the whole sequence. Thus the length of the period  $t_0$  to  $t_1$  represents the charge  $Q_{\text{GS}}$  consumed by the gate-to-source capacitance, whilst the length of the period  $t_2$  to  $t_3$  represents the charge  $Q_{\text{GD}}$  consumed by the gate-to-drain or “Miller” capacitance. The total charge at time  $t_3$  is the charge required to switch the given voltage  $V_{\text{DD}}$  and current  $I_D$ . The additional charge consumed after time  $t_3$  does not represent “switching” charge; it is simply the excess charge which will be delivered by the drive circuit because the amplitude of the applied gate drive voltage normally will be higher (as a matter of good design practice) than the bare minimum required to accomplish switching.

 


Figure 4. Basic Gate Charge Test Circuit

#### 4. Beware When Comparing Different Products

Manufacturers sometimes make technical claims for their products that appear to be plausible, but which in actuality do not stand up to scrutiny. A case in point concerns the input capacitance of a power MOSFET. Statements such as “the input capacitance of device Y is less than that of device X, ergo Y is a faster switch than X”, are frequently bandied about, but are just as frequently erroneous. Apart from the obvious speciousness of many such statements — “apples” are frequently not compared with “apples”, and obviously larger chips have more self capacitance than smaller ones—the more basic fundamentals are generally overlooked. As this application note shows, of “bottom line” importance is the total gate charge required for switching. The lower the charge, the lower is the gate drive current needed to achieve a given switching time.

A general comparison between hypothetical MOSFETs brands “X” and “Y” is illustrated in the Figure. Device X has a higher input capacitance; hence the initial slope of its gate charge characteristic is less than that of device Y.  $Q_{GS}$  of device X is, however, about the same as that of device Y, because it has a higher transconductance and therefore requires less voltage on its gate for the given amount of drain current ( $V_{GX}$  is less than  $V_{GY}$ ). The “Miller” charge consumed by device X is considerably less than that consumed by device Y. The overall result is that the total charge required to switch device X,  $Q_X$ , is considerably *less* than that required to switch device Y,  $Q_Y$ . Had the comparison between devices X and Y been made on the more superficial basis of input capacitances, it would have been concluded— erroneously—that Y is “better” than X. Another consideration is the energy required for switching. Again, device X scores handsomely over device Y in this example. The energy is the product of the gate charge and the gate voltage, and is represented by the area of the rectangle whose corner lies at the “switching point”. (Point 1 for device X, and point 2 for device Y.) It is obvious that X requires significantly less gate energy than Y. To summarize: beware of superficial comparisons. Check the full facts before deciding which MOSFET really has the edge in switching performance.

#### Related Topics:

*Gate drive considerations for IGBT modules*

*Gate drive characteristics of IGBTs*

*Gate drive requirements of MOS-gated transistors*

*High-voltage gate drive ICs*

*Three-phase gate drive IC*

*Gate drive IC for ballasts*

*Transformer-isolated gate driver*

 


Figure 5. Basic Gate Charge Waveforms

 


Figure 6. Comparison of Gate Charge Characteristics of Different Device Types.

International  
**IOR** Rectifier

**WORLD HEADQUARTERS:** 233 Kansas St., El Segundo California 90245, Tel: (310) 322 3331

**EUROPEAN HEADQUARTERS:** Hurst Green, Oxted, Surrey RH8 9BB, UK Tel: ++ 44 1883 732020

**IR CANADA:** 7321 Victoria Park Ave., Suite 201, Markham, Ontario L3R 2Z8, Tel: (905) 475 1897

**IR GERMANY:** Saalburgstrasse 157, 61350 Bad Homburg Tel: ++ 49 6172 96590

**IR ITALY:** Via Liguria 49, 10071 Borgaro, Torino Tel: ++39 11 451 0111

**IR FAR EAST:** K&H Bldg., 2F, 3-30-4 Nishi-Ikeburo 3-Chrome, Toshima-Ki, Tokyo Japan 171 Tel: 81 3 3983 0086

**IR SOUTHEAST ASIA:** 315 Outram Road, #10-02 Tan Boon Liat Building, Singapore 0316 Tel: 65 221 8371

Data and specification subject to change without notice.